



UNITED INTERNATIONAL UNIVERSITY (UIU)

Dept. of Computer Science & Engineering

Course No: EEE 2123

Title: Electronics

Trimester: Summer 2023

Section: B

Class Test -3

Total Marks: 20

Time: 25 minutes



Name:

ID:

Q1.

Determine and draw V_o for the given network:

[10]

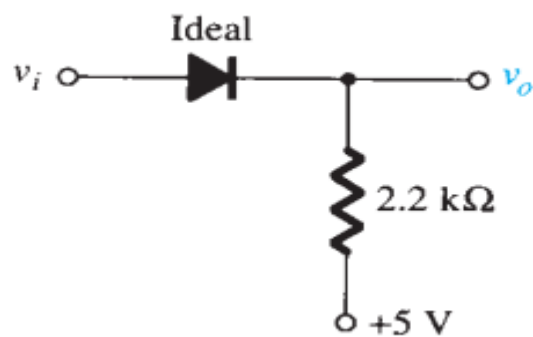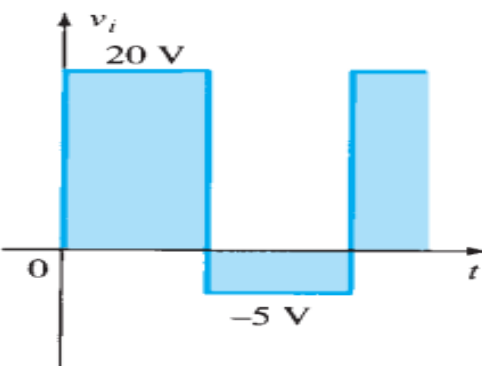

Q2.

Determine and draw V_o for the given network:

[10]

