

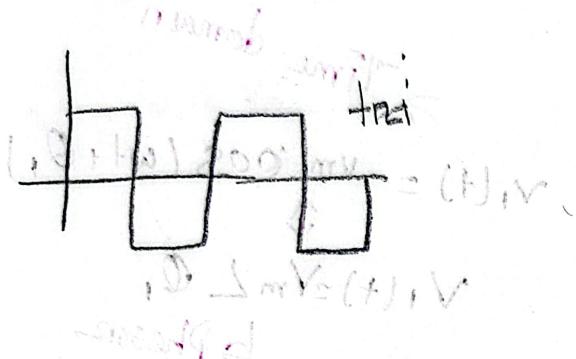
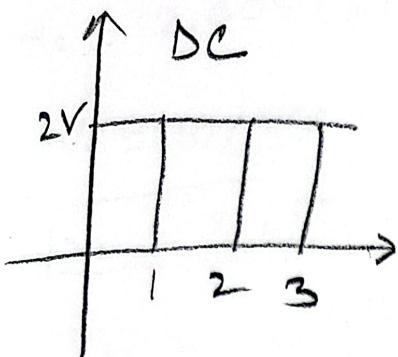
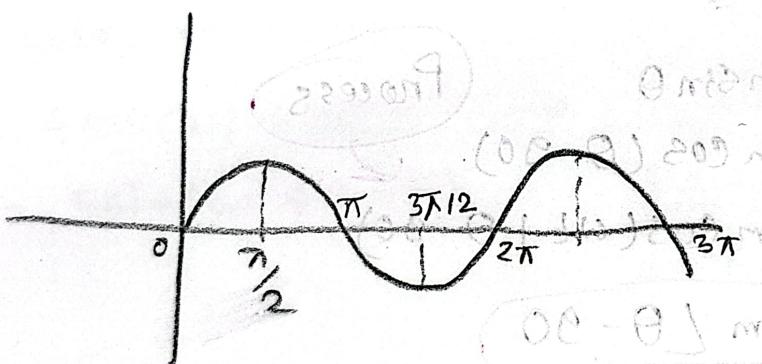


AC circuit

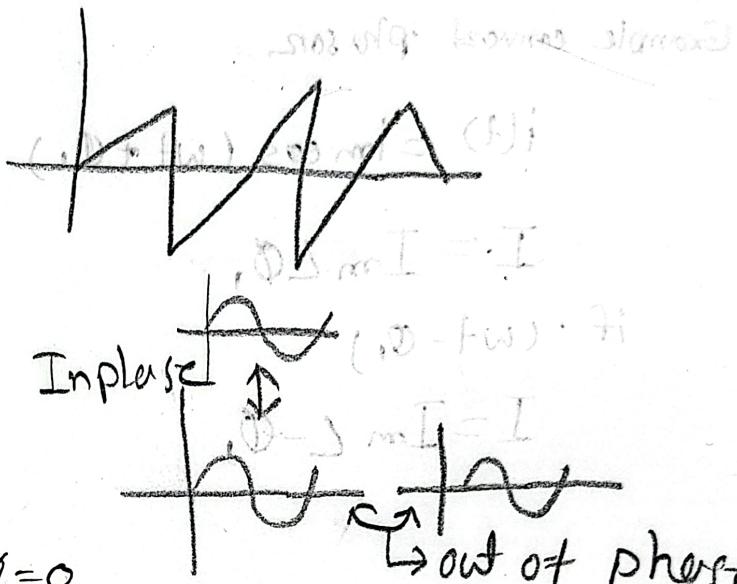

$$V = V_m \sin(\omega t + \phi)$$
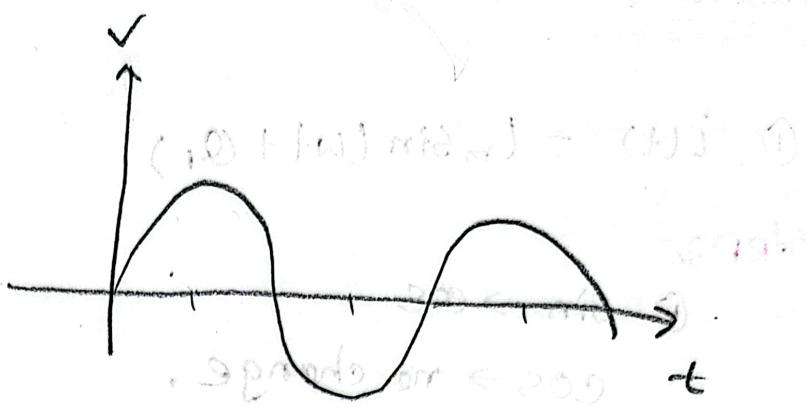
$$V = V_m \sin(\omega t + \phi), \phi = 0$$




* $\sin(\omega t + \phi) \theta \rightarrow -\theta,$

$\sin(\omega t - \phi) \theta \rightarrow +\theta,$

$\theta = 0 \rightarrow 0$

$$V = V_m \sin(\omega t + \phi)$$

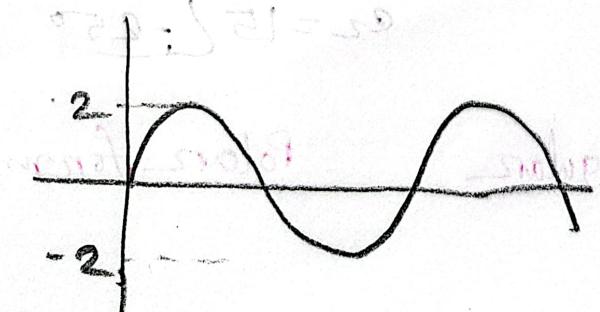

phasor / frequency domain

$$\textcircled{1} \quad i(t) = I_m \sin(\omega t + \phi_1)$$

Step 2

\textcircled{1} Sin \rightarrow Cos

Cos \rightarrow no change.

Example convert phasor

$$i(t) = I_m \cos(\omega t + \phi_1)$$

$$I = I_m \angle \phi_1$$

$$\text{if } (\omega t - \phi_1)$$

$$I = I_m \angle -\phi_1$$

$$v_i(t) \xrightarrow{\text{Time domain}} v_m \cos(\omega t + \phi_1)$$

$$v_i(t) \xleftarrow{\text{Phasor}} V_m \angle \phi_1$$

$$\boxed{\sin \theta = (\phi - \cos(\theta - 90^\circ))}$$

Q.1

$$V_m \sin(\omega t + \theta) \rightarrow V_m \sin \theta$$

$$\Rightarrow V_m \cos(\theta - 90^\circ)$$

$$\Rightarrow V_m \cos(\omega t + \theta - 90^\circ)$$

$$\Rightarrow \boxed{V_m \angle \theta - 90^\circ}$$

Process

Complex number

$$x + iy \quad / \cdot a + ib$$

real

imaginary

$$c_1 = 20 \angle 90^\circ$$

$$c_2 = 15 \angle -25^\circ$$

complex number rectangular form

$$3 + i8$$

Polar form

$$v_1 = 10 \cos(\omega t + 70^\circ)$$

$$v_2 = 2 \cos(\omega t + 50^\circ)$$

$$v_1 = 10 \angle 70^\circ$$

$$\boxed{v_1 = 2 \angle 50^\circ}$$

$$v_2 = 2 \angle 0 - 50^\circ$$

$$v = v_1 + v_2$$

$$30^\circ (10 \cos(\omega t + 70^\circ) + 2 \cos(\omega t + 0 - 50^\circ))$$

$$10 \sin(\omega t + 70^\circ) + 2 \sin(\omega t + 0 - 50^\circ)$$

$$\boxed{2 \angle 0 - 90^\circ}$$

$$10 \cos(\omega t + 70^\circ) + 2 \cos(\omega t + 0 - 50^\circ)$$

$$5 \angle -20^\circ - 90^\circ$$

$$v = -4 \angle 50 - 90^\circ$$

$$\rightarrow -5 \sin(\omega t + 50^\circ)$$

$$5 \cos(\omega t + 50^\circ)$$

rectangular to polar:

$$i_1 = 4 \cos(\omega t + 30^\circ) \rightarrow 4 \angle 30^\circ - 0^\circ$$

$$i_2 = 5 \sin(\omega t + 0 - 20^\circ) \\ 5 \angle -20 - 90^\circ \\ = 5 \angle -110^\circ - 0^\circ$$

$$I = i_1 + i_2 = 4 \angle 30^\circ + 5 \angle -110^\circ$$

$$= 3.21 \angle -56.97^\circ$$

polar to rect

4.

② ~~45°~~

$$(40 \angle 50^\circ + 22 - 30^\circ)^{1/2}$$

$$40 \angle 50^\circ \cdot 40(\cos 50^\circ + j \sin 50^\circ)$$

$$= 25.71 + j 30.64$$

$$2 \angle -30^\circ$$

$$= 20[\cos(-30) + \sin(-30)j]$$

$$= 17.32 - j 10$$

$$(0.8 + (\cancel{43.03} + \cancel{j 20.64}))^2$$

$$43.03 + j 20.64$$

Lead / Lag / Leading

$$v_1 = -10 \cos(\omega t + 50^\circ)$$

$$v_2 = 12 \sin(\omega t - 10^\circ)$$

$$v_1 = 10 \cos(\omega t + 50^\circ - 180^\circ)$$

$$= 10 \cos(\omega t - 130^\circ)$$

$$\begin{aligned} v_2 &= 12 \cos(\omega t - 10^\circ - 90^\circ) \\ &= 12 \cos(\omega t - 100^\circ) \end{aligned}$$

here, v_2 is leading

v_1 is lagging

$$2\pi f \times 0.2 = \omega$$

$$2\pi \times 60 \times 0.2 = \omega$$


$$1.2 = \omega$$

5 similar graphs

$$-\cos(\omega t) \leftarrow \cos(\omega t + 180^\circ)$$

$$0 \rightarrow + \rightarrow \text{leading}$$
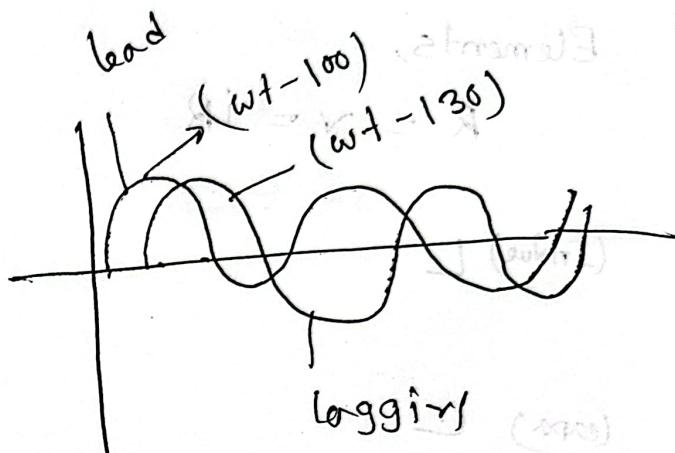
$$0 \rightarrow - \rightarrow \text{lagging}$$



$$(v_2 + 10) \sin(\omega t) = \sin(\omega t \pm 180^\circ)$$

$$I \sin \omega t = V$$

$$\frac{V}{I \omega t} = I$$

$$I = \frac{V}{R}$$

$$I = \frac{V}{R \times 0.25}$$

Capacitance, Inductance, Impedance


~~Inductance~~ ~~Capacitance~~

↳ Inductance \rightarrow Re., $V = IR \rightarrow V = I(\omega L)$

↳ Capacitance (complex) \rightarrow

Elements,

$$R = \frac{V}{I} = iR$$

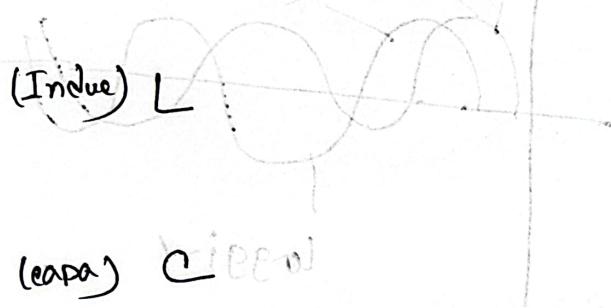

Frequency / Phasor

$$V = RI \rightarrow V = R\left(\frac{V}{I}\right) \rightarrow V = R^2 I$$

$$V = IZ = Ij\omega L$$

$$V = IZ = I \cdot \frac{1}{j\omega C}$$

Expt

(9.8)

$$V = 12 \cos(60t + 45^\circ)$$

phasor diagram

$$V = j\omega L I$$

$$I = \frac{V}{j\omega L}$$

$$= \frac{12 \angle 45^\circ}{j60 \times 0.1}$$

$$= \frac{12 \angle 45^\circ}{6j}$$

$$= 2 \angle -45^\circ$$

$$= 2 \cos(60t - 45^\circ)$$


$$j = j \text{ (imaginary unit)}$$

$$\omega = 60 \text{ rad/s}$$

$$\theta = 12 \angle 45^\circ$$

$$L = 0.1$$

Example 9.9

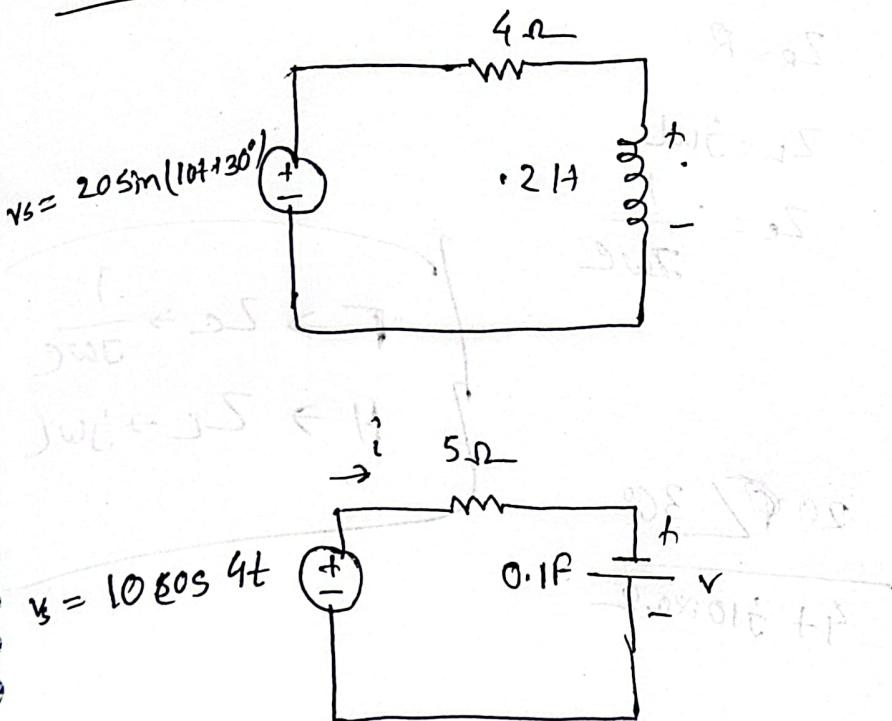

$$\textcircled{1} T_0 \rightarrow P_D$$

$$\textcircled{2} R - 2\Omega$$

$$C \rightarrow Z_C$$

$$L \rightarrow Z_L$$

$$\sqrt{s} = 10 \angle 0^\circ$$

$$I = \frac{\gamma}{Z_{eq}}$$

$$\omega = 4$$

$$= \frac{10 \angle 0^\circ}{5 - 2.5j}$$

$$R = 5$$

$$1.789 \angle 26.566^\circ$$

$$C = 0.1\text{F}$$

$$SI = 91 \text{ A}$$

$$Z_{eq} = \frac{1}{j\omega C}$$

$$V = I Z_C$$

$$= \frac{1}{j4 \times 0.1}$$

$$= 1.789 \angle 26.566^\circ \times (-2.5j)$$

$$= \frac{1}{j4}$$


$$= 4.47 \angle -63.43^\circ$$

$$= -j2.5$$

$$i(t) = 1.789 \cos(4t - 26.56^\circ)$$

$$v_C(t) = 4.47 \cos(4t + 63.43^\circ)$$

$$20 \sin(10t + 30^\circ)$$

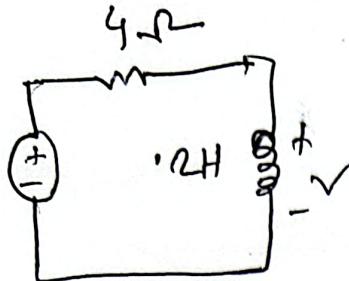

$$Z_R = R$$

$$Z_L = j\omega L$$

$$Z_C = \frac{1}{j\omega C}$$

$$F \rightarrow Z_C \rightarrow \frac{1}{j\omega C}$$

$$H \rightarrow Z_L \rightarrow j\omega L$$

$$I_2 = \frac{V}{Z_{eq}}$$

$$= \frac{V}{Z_R + Z_L}$$

$$20 \angle 30^\circ$$

$$4 + j10 \times 0.2$$

$$= \frac{20}{4 + j2.0}$$

$$= 4.97 \angle 3.4^\circ$$

$$= 4.97 \sin(10t + 3.4^\circ)$$

$$V_2 I R = I_2$$

$$\approx (4.97 \angle 3.4^\circ) (j10 \times 0.2)$$

$$m \rightarrow 10^{-3}$$


$$\mu \rightarrow 10^{-6}$$

$$n \rightarrow 10^6$$

$$\kappa \rightarrow 10^3$$

$$m \rightarrow 10^6$$

* Find $v_o(t)$

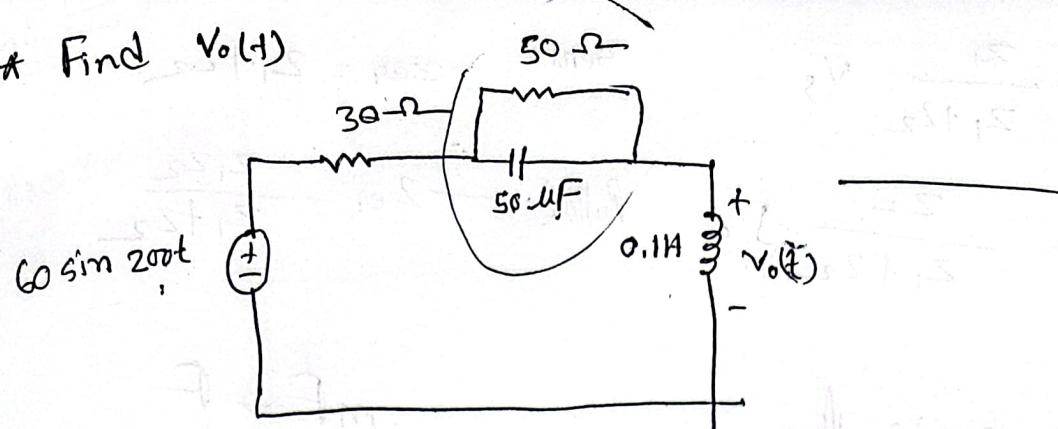

① Z_{eq}

$$Z_{eq} = \frac{50 \times 0.1}{50 + 30} = \frac{5}{8} \Omega$$

$$100 \times 0.08 = 8$$

$$\frac{1}{2} + \frac{1}{2}$$

$$u \rightarrow f$$

$$x \times 10^{-6}$$

$$\frac{1}{50} + \frac{1}{200 \times 50 \times 10^{-6}}$$

$$100 L - 89.98$$

$$\frac{1}{50 + \frac{1}{200 \times 50 \times 10^{-6}}}$$

Xc

80.50 = 80.50

carnovas®
Nebivolt

$$VDR \rightarrow V_1 = \frac{Z_1}{Z_1 + Z_2} V_s$$

$$CDR \rightarrow I_1 = \frac{Z_2}{Z_1 + Z_2} I_s$$


$$\text{Series } Z_{eq} = Z_1 + Z_2$$

$$\text{Parallel } Z_{eq} = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

Q.7

Impedance Combination

$$mF \xrightarrow{10^{-3}} F$$

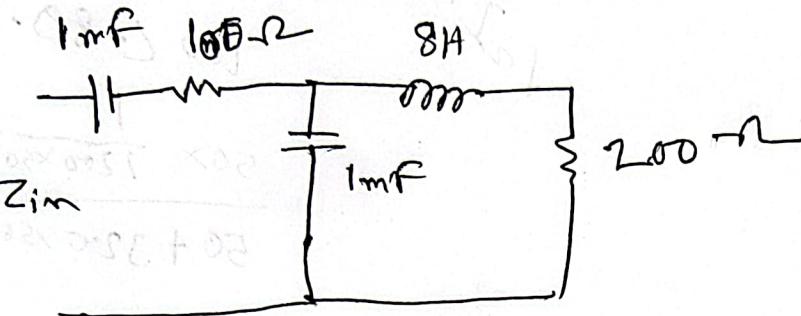

$$\omega = 10 \text{ rad/s}$$

$$R = Z_R = 100\Omega$$

$$L \rightarrow Z_L = j\omega L$$


$$= (10 \times 80)j \\ = j80\Omega$$

$$C \rightarrow Z_C \rightarrow \frac{1}{j\omega C} \\ = \frac{1}{j10 \times 1 \times 10^{-3}}$$

$$\text{Parallel } Z = -j100\Omega$$

$$\frac{(-j100) \times (200 + j80)}{-j100\Omega + 200 + j80}$$




$$= 107.16 \angle -62.48^\circ$$

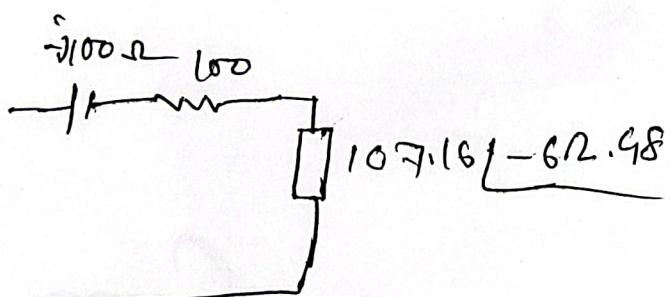

$$\therefore Z_{in} = -j100\Omega + 100 + 107.16 \angle -62.48^\circ$$

$$= 245.75 \angle -52.52^\circ$$

Q.11 P.P

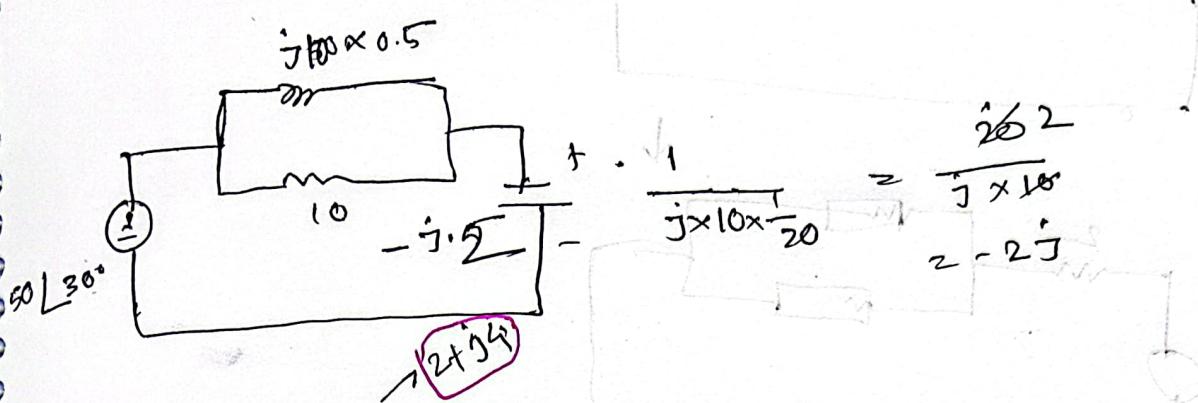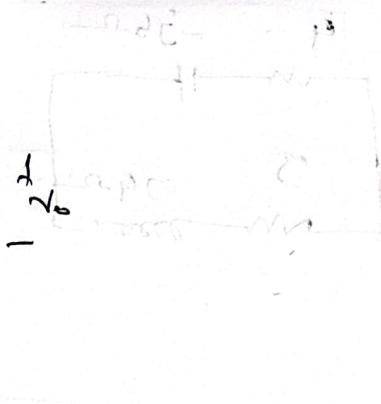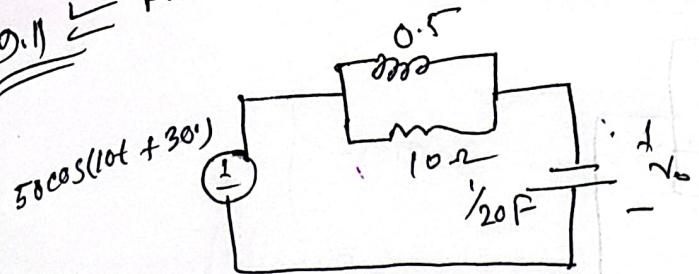

$$Z_{eq} = \frac{10 \times j5}{(10 \times j5)(j10 - j2)} = 2 + 2j$$


$$I = \frac{50\angle 30^\circ}{2 + 2j} = \frac{50\angle 30^\circ}{2.82 \angle 45^\circ} = 17.73 \angle -15^\circ$$

$$\therefore V = I Z_e = 17.73 \angle -15^\circ \times (-j2) \\ = 35.46 \angle -105^\circ$$

$$\therefore 35.46 \cos 110t + (05^\circ) V.$$



Q.12

$120 \angle 10^\circ$

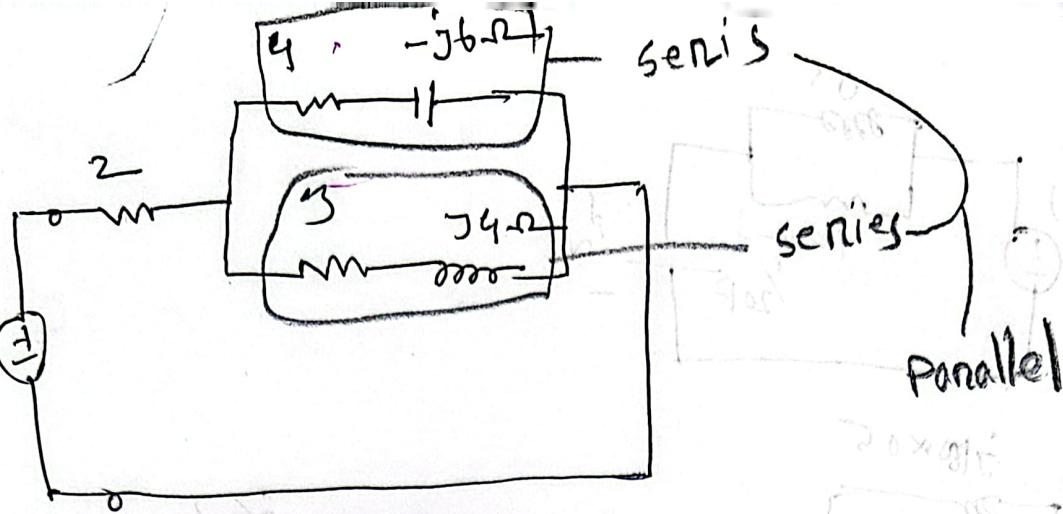

Exp - Q. 9, 10, 11
P.P - Q. 9, 10, 11
39, 41, 42, 43, 46, 48, 50, 52

$120 \angle 10^\circ$

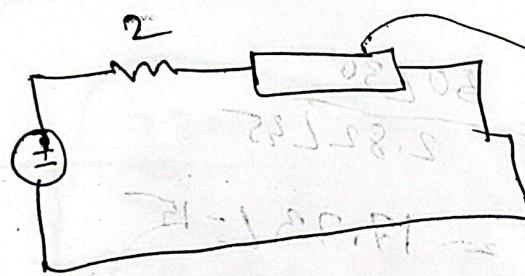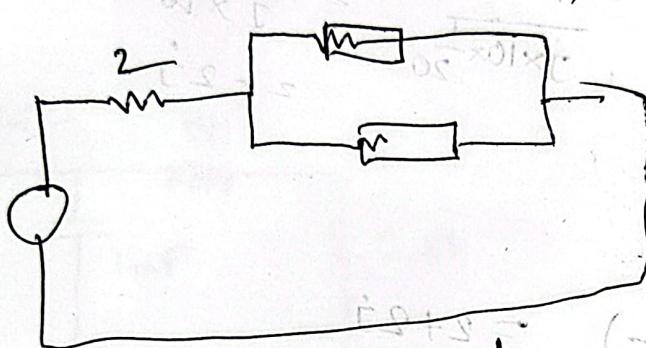

$$\frac{(4-j6)(3+j4)}{(4-j6)+(3+j4)}$$

$$= 9.83 + 1.09j$$

$$6.83 + 1.09j$$

$$Z_T = 4.83 + 1.09j + 2$$

$$= 6.83 + 1.09j$$



$$\therefore I = \frac{V}{Z_T} = \frac{120 \angle 10^\circ}{6.83 + 1.09j}$$

$$\Rightarrow rL\theta = 6.91 \angle 9.06^\circ$$

$$2 \angle 17.41 \angle 10^\circ$$


$$= 17.36 \angle 0.94^\circ$$

Thevenin

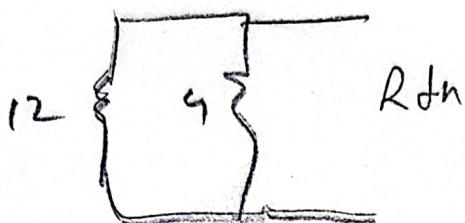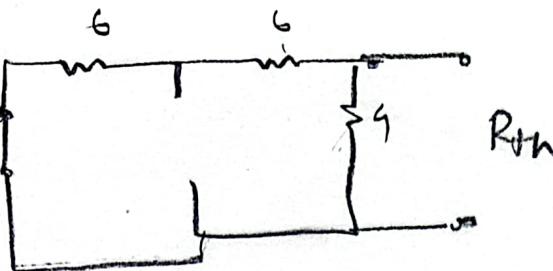


$$\frac{12 \times 9}{16} = 3 \Omega$$

max power in $1A$ eq

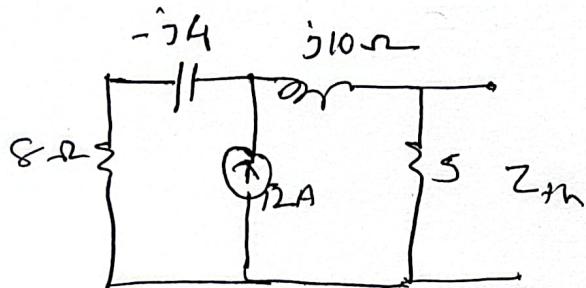

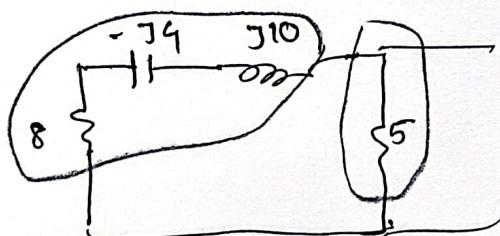
$$Z_m = \frac{(8 - j4 + j10) \times 5}{5 + 8 - j6}$$



11.4 avg, x_{rms}

$$x_{avg} = \frac{1}{T} \int_0^T x(t) dt$$

area

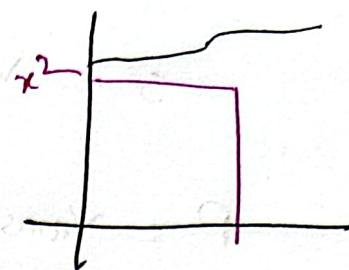


$$x_{avg} = \frac{1}{T} \int_0^T x^2(t) dt$$

Sine-wave,

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$V_{avg} = 0$$

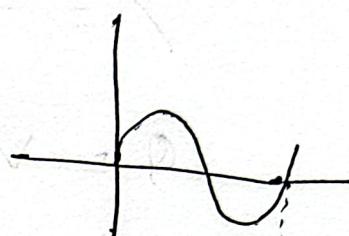

$$R_1 \angle \theta_1 \times R_2 \angle \theta_2$$

$$R_1 R_2 \angle \theta_1 + \theta_2$$

$$= x + iy$$

Power

DC

$$P = VI$$

AC

$$P = V(t) \cdot i(t)$$

$$V = V_m \angle \theta_v$$

$$I = I_m \angle -\theta_i$$

- apparent power (S)
- real power (P)
- reactive power (Q)

$$P = VI = (V_m \angle \theta_v) (I_m \angle -\theta_i)$$

$$= V_m I_m \angle \theta_v - \theta_i$$

$$= V_m I_m \cos(\theta_v - \theta_i)$$

$$+ j V_m I_m \sin(\theta_v - \theta_i)$$

carnovas®
Nebivolol

115 Apparent Power. $S = P + jQ \xrightarrow{\text{real part}} \text{real power}$


$$S = V_{\text{rms}} \cdot I_{\text{rms}} \cos(\theta_v - \theta_i)$$

$$P = V_{\text{rms}} \cdot I_{\text{rms}} \cos(\theta_v - \theta_i)$$

$$= \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

$$Q = V_{\text{rms}} I_{\text{rms}} \sin(\theta_v - \theta_i)$$
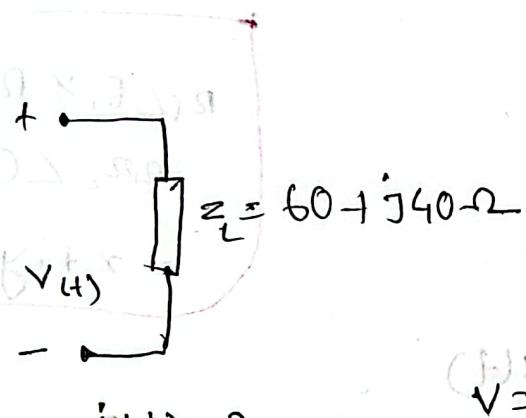
$$= \frac{V_m I_m}{2} \sin(\theta_v - \theta_i)$$



$$V_u = 320 \cos(377t + 10^\circ)$$

$$V = I R \Rightarrow I = \frac{V}{R_L}$$

$$(2) \frac{320 \angle 10^\circ}{60 + j40}$$

$$(3) \quad \text{Ans}$$

$$(4) \quad z = 4.43 \angle -23.7^\circ A$$

$$= 4.43 \cos(377t - 23.7^\circ)$$

$$P_L = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) \quad Q_L$$

$$= \frac{320 \times 4.43}{2} \cos(10 + 23.7^\circ)$$

$$= \frac{320 \times 4.43}{2} \sin(10 + 23.7^\circ)$$

$$= 5.89.68 \omega$$

$$= 393.27 \text{ var}$$

$$S_L = P + jQ = |S_L| = \sqrt{P^2 + Q^2}$$

$$= \frac{V_m I_m}{2} = V_{rms} I_{rms}$$

$$= \frac{320 \times 4.43}{2}$$

11.4, 11.5

Branch - 11.9 - 11'10

PP - 11.9 - 16'10

Ex - 38, 39, 41

$$P_f = \cos(\theta_r - \theta_i)$$

$$= \cos(10 + 23.7)$$

$$= 0.83$$